

CSCI 4120 Computer-Aided Design of Very Large Scale Integrated Circuits

Homework 1 (Part A)

Due Date: Feb 17, 2025 11:59pm

1. Given that  $\forall x F = Fx \cdot Fx'$  and  $\exists x F = Fx + Fx'$ :
  - (a) Prove that  $\forall x y F = Fxy \cdot Fxy' \cdot Fx'y \cdot Fx'y'$
  - (b) Prove that  $\exists x y F = Fxy + Fxy' + Fx'y + Fx'y'$
  - (c) What is  $\forall x \exists y F$ ? Prove your answer.
2. The Unate Recursive Paradigm (URP) is to determine tautology of a Boolean equation available as a SOP cube list. The idea can be extended to do unate recursive complement since  $\bar{f} = x\bar{f}_x + x'\bar{f}_{x'}$ 
  - (a) Show by hand a recursion tree for the algorithm URP Complement, running on the function  $F(x, y, z, w) = \bar{x}yz + \bar{x}\bar{z}w + xyz$
  - (b) Show with a simple Karnaugh map that your answer for the complement in part (i) is correct.
3. A simple comparator takes two 2-bit unsigned binary numbers  $a_1a_0$  and  $b_1b_0$ , and compares their magnitude, and sets the output  $z = 1$  when  $a_1a_0$  is larger than or equal to  $b_1b_0$ .
  - (a) Write the Boolean function for  $z$ .
  - (b) Construct an ROBDD (Reduced Order Binary Decision Diagram) for  $z$  with a good variable ordering.
4. Show how you can build a BDD for the Boolean function  $F = a \oplus \bar{b}$  using the ITE recursion.
5. Consider a 2-level circuit  $C$  representing the following Boolean function:

$$F = a'c' + a'bc + ac'd + ab'd$$

- (a) How many literals are there in this 2-level circuit  $C$ ?
- (b) Draw a Karnaugh map for the function  $F$ .
- (c) Which of the cubes (product terms) are prime?
- (d) Which of the cubes are redundant?
- (e) Show how the 3 steps of *Expand*, *Irredundant* and *Reduce* can be applied to  $F$  to obtain an equivalent 2-level circuit  $C'$  with the minimum number of literals.


Yu Ching Hei 1155193237

$$\begin{aligned}
 1(a) \quad \forall xy F &= \forall x (\forall y F) \\
 &= \forall x (F_y \cdot F_{\bar{y}}) \\
 &= x (F_y \cdot F_{\bar{y}}) \cdot \bar{x} (F_y \cdot F_{\bar{y}}) \\
 &= F_{xy} \cdot F_{x\bar{y}} \cdot F_{\bar{x}y} \cdot F_{\bar{x}\bar{y}}
 \end{aligned}$$

$$\begin{aligned}
 1(c) \quad \forall x \exists y F &= \forall x (F_y + F_{\bar{y}}) \\
 &= x (F_y + F_{\bar{y}}) \cdot \bar{x} (F_y + F_{\bar{y}}) \\
 &= (F_{xy} + F_{x\bar{y}}) \cdot (F_{\bar{x}y} + F_{\bar{x}\bar{y}})
 \end{aligned}$$

$$\begin{aligned}
 1(b) \quad \exists xy F &= \exists x (\exists y F) \\
 &= \exists x (F_y + F_{\bar{y}}) \\
 &= x (F_y + F_{\bar{y}}) + \bar{x} (F_y + F_{\bar{y}}) \\
 &= F_{xy} + F_{x\bar{y}} + F_{\bar{x}y} + F_{\bar{x}\bar{y}}
 \end{aligned}$$
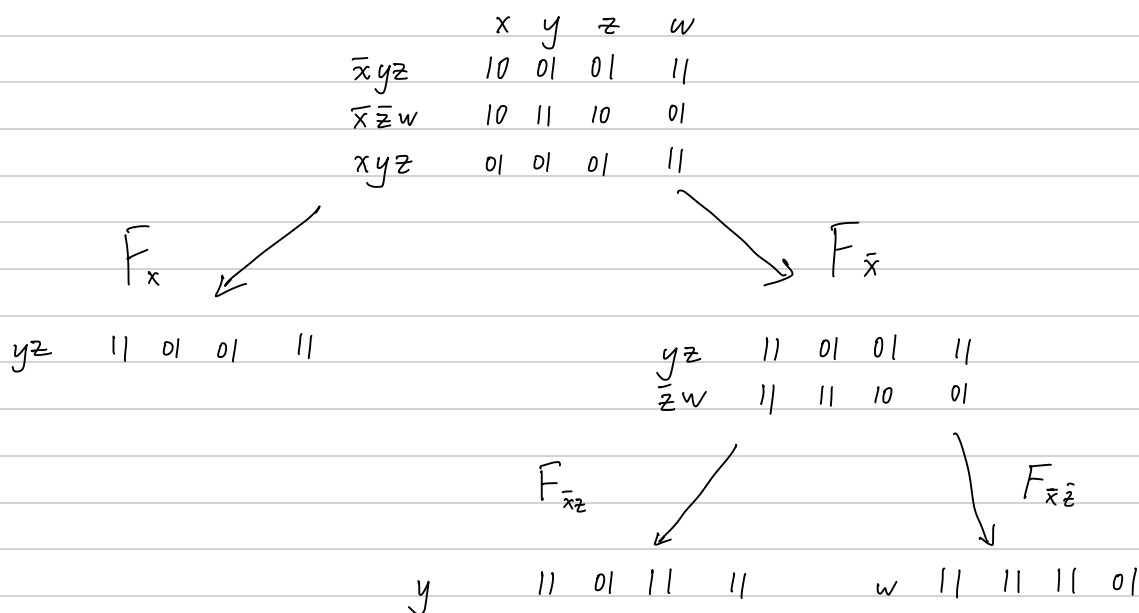
$$2(a) \quad F(x, y, z, w) = \bar{x}yz + \bar{x}\bar{z}w + xyz$$



It is not a tautology and

$$F_x = yz, F_{\bar{x}z} = y, F_{\bar{x}\bar{z}} = w, \forall z F_{\bar{x}} = F_{\bar{x}z} \cdot F_{\bar{x}\bar{z}}$$

By Shannon Expansion wrt.  $z$ , we have

$$\begin{aligned}
 \overline{F_{\bar{x}}} &= z \overline{F_{\bar{x}z}} + \bar{z} \overline{F_{\bar{x}\bar{z}}} \\
 &= z \bar{y} + \bar{z} \bar{w}
 \end{aligned}$$

And from URP, we have

$$\overline{F_x} = \overline{yz} = \bar{y} + \bar{z}$$

And

$$\begin{aligned}
 \overline{F} &= x \overline{F_x} + \bar{x} \overline{F_{\bar{x}}} \\
 &= x(\bar{y} + \bar{z}) + \bar{x}(z\bar{y} + \bar{z}\bar{w}) \\
 &= x\bar{y} + x\bar{z} + \bar{x}z\bar{y} + \bar{x}\bar{z}\bar{w}
 \end{aligned}$$

2(b) K-Map for  $\bar{F}$  in (a)

$$\bar{F} = x\bar{y} + x\bar{z} + \bar{x}\bar{y}z + \bar{x}\bar{z}w$$

$\begin{matrix} \swarrow zw \\ xy \end{matrix}$	00	01	11	10
00	1	0	1	1
01	1	0	0	0
11	1	1	0	0
10	1	1	1	1

K-Map for  $F$

$$F = \bar{x}yz + \bar{x}\bar{z}w + xyz$$

$\begin{matrix} \swarrow zw \\ xy \end{matrix}$	00	01	11	10
00	0	1	0	0
01	0	1	1	1
11	0	0	1	1
10	0	0	0	0

$\therefore$  Complement in (a) is correct.



3(a)

$$a > b \Rightarrow a_1\bar{b}_1 + a_0\bar{b}_0a_1 + a_0\bar{b}_0\bar{b}_1$$

$$a = b \Rightarrow \bar{a}_1a_0\bar{b}_1\bar{b}_0 + \bar{a}_1a_0\bar{b}_1b_0 + a_1a_0b_1b_0 + a_1a_0\bar{b}_1\bar{b}_0$$

$$\begin{aligned} z &= "a > b" + "a = b" \\ &= a_1\bar{b}_1 + a_0\bar{b}_0a_1 + a_0\bar{b}_0\bar{b}_1 \\ &\quad + \bar{a}_1a_0\bar{b}_1\bar{b}_0 + \bar{a}_1a_0\bar{b}_1b_0 + a_1a_0b_1b_0 + a_1a_0\bar{b}_1\bar{b}_0 \\ &= a_1\bar{b}_1 + (a_0\bar{b}_0a_1 + a_0\bar{b}_0\bar{b}_1) \\ &\quad + \bar{a}_1\bar{b}_1(\bar{a}_0\bar{b}_0 + a_0b_0) + a_1b_1(\bar{a}_0\bar{b}_0 + a_0b_0) \\ &= a_1\bar{b}_1 + (a_0\bar{b}_0a_1 + a_0\bar{b}_0\bar{b}_1) \\ &\quad + (\bar{a}_1\bar{b}_1 + a_1b_1)(\bar{a}_0\bar{b}_0 + a_0b_0) \\ &= a_1\bar{b}_1 + (a_0\bar{b}_0a_1 + a_0\bar{b}_0\bar{b}_1) + (a_1\bar{b}_1 + a_1b_1)(a_0\bar{b}_0 + a_0b_0) \end{aligned}$$

(b)

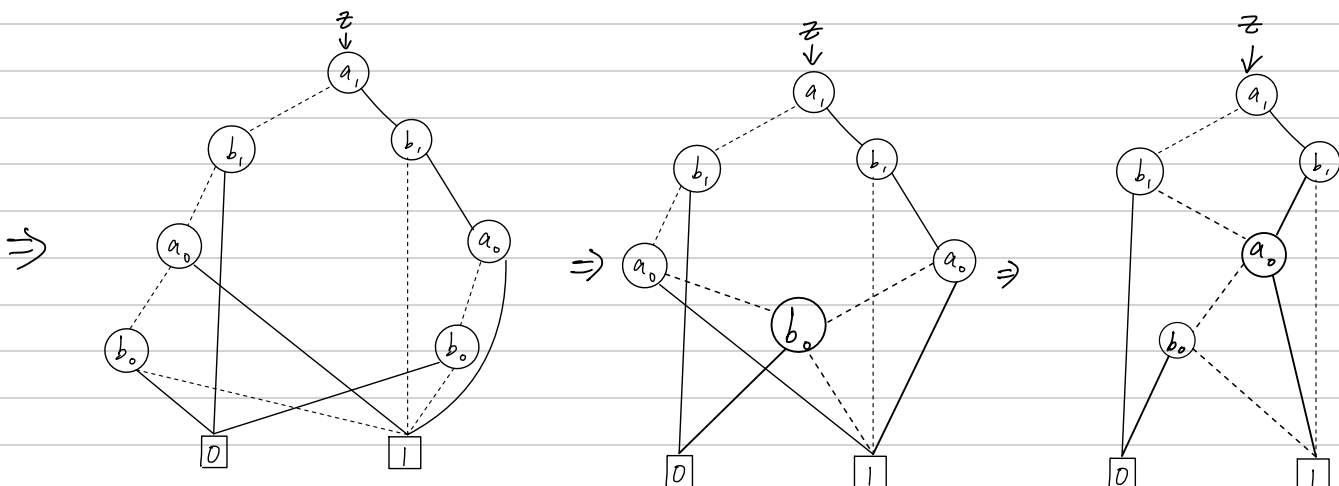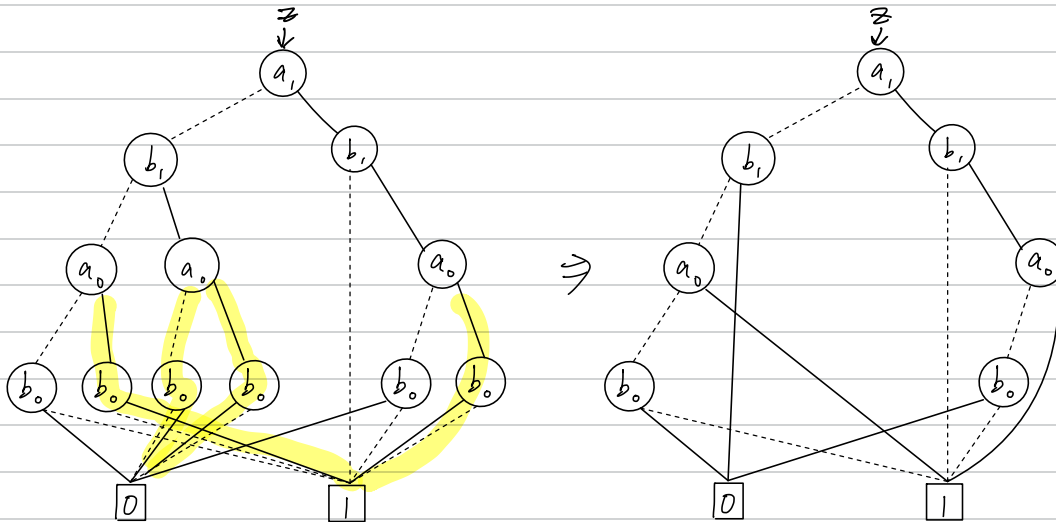

Q4

$$F = a \oplus b$$

assume  $A$  and  $B$  are simple BDD of

$$a \oplus b : \text{ITE}(A, B, \bar{B})$$

↓  
assume  $A > B$

↓  
let  $x = a$  which is root of  $A$

$$\text{PosFac} = \text{ITE}(1, B, \bar{B})$$

$$\text{NegFac} = \text{ITE}(0, B, \bar{B})$$

$R$  = new node lab'd by  $a$

$$R.\text{low} = \text{NegFac}$$


$$= \text{ITE}(0, B, \bar{B})$$

↳ return  $\bar{B}$


$$R.\text{high} = \text{PosFac}$$

$$= \text{ITE}(1, B, \bar{B})$$

↳ return  $B$

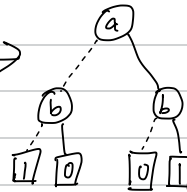

$$A = a$$

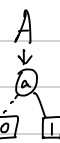


$$\text{and } B = b$$




Then implies

$$\bar{B} = \bar{b}$$

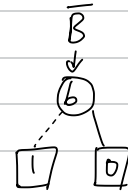

Simplify ( $R$ )

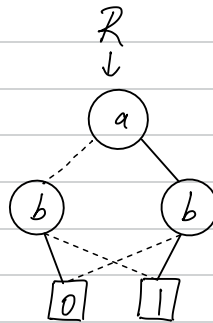

⇒ return  $R$

↓

(a) 11

(b)	$\begin{matrix} ab \\ \backslash \\ cd \end{matrix}$	00	01	11	10
	00	1	1	0	0
	01	1	1	1	1
	11	0	1	0	0
	10	0	1	1	0

(c)  $a'c', ab'd$

(d)  $ac'd, a'bc$

(e) By ESPRESSO Algorithm

Expansion

1) Build a OFF set of F

$$F = a'c' + a'b'c + ac'd + ab'd$$

URP

	a	b	c	d
$a'c'$	10	11	10	11
$a'b'c$	10	01	01	11
$ac'd$	01	11	10	01
$ab'd$	01	10	11	01

$F_c$

$F_{\bar{c}}$

$a'b$	10	01	11	11
$ab'd$	01	10	11	01

$F_{ca}$

$F_{c\bar{a}}$

$a'$	10	11	11	11
$ad$	01	11	11	01
$ab'd$	01	10	11	01

$F_{\bar{c}a}$

$F_{\bar{c}\bar{a}}$

$b'd$	11	10	11	01
-------	----	----	----	----

$b$	11	01	11	11
-----	----	----	----	----

$d$	11	11	11	01
$b'd$	11	10	11	01

11 11 11 11  $\Rightarrow$  Tautology

$$\begin{aligned}\bar{F}_c &= a\bar{F}_{ca} + \bar{a}\bar{F}_{c\bar{a}} \\ &= a(\bar{b}\bar{d}) + \bar{a}\bar{b} \\ &= ab + a\bar{d} + \bar{a}\bar{b}\end{aligned}$$

$$\begin{aligned}\bar{F}_{\bar{c}} &= a\bar{F}_{\bar{c}a} + \bar{a}\bar{F}_{\bar{c}\bar{a}} \\ &= a(\bar{d} + \bar{b}\bar{d}) + \bar{a}(1) \\ &= a(\bar{d}(1 + \bar{b})) \\ &= a\bar{d}\end{aligned}$$

$$\begin{aligned}\bar{F} &= c\bar{F}_c + \bar{c}\bar{F}_{\bar{c}} \\ &= abc + ac\bar{d} + \bar{a}\bar{b}c + a\bar{c}\bar{d}\end{aligned}$$

K-Map of  $\bar{F}$

$ab \backslash cd$	00	01	11	10
00	0	0	1	1
01	0	0	0	0
11	1	0	1	1
10	1	0	0	1


K-Map of F

$ab \backslash cd$	00	01	11	10
00	1	1	0	0
01	1	1	1	1
11	0	1	0	0
10	0	1	1	0

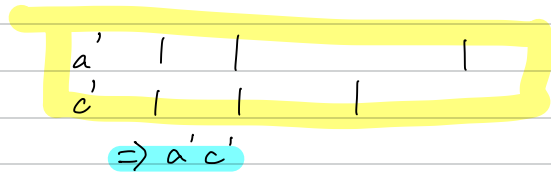
2) Expand 4 cubes

$$F = a'c' + a'bc + ac'd + ab'd$$


$abc \quad ac\bar{d} \quad \bar{a}\bar{b}c \quad a\bar{c}\bar{d}$



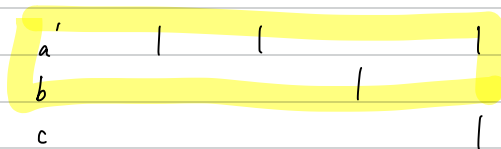
$abc \quad ac\bar{d} \quad \bar{a}\bar{b}c \quad a\bar{c}\bar{d}$



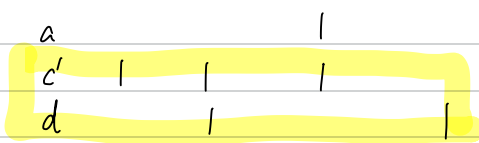$abc \quad ac\bar{d} \quad \bar{a}\bar{b}c \quad a\bar{c}\bar{d}$



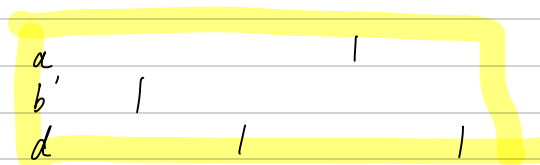$abc \quad ac\bar{d} \quad \bar{a}\bar{b}c \quad a\bar{c}\bar{d}$



Expansion form would be

$$F = a'c' + c'd + a'b + ab'd$$

K-Map of F

$ab \backslash cd$	00	01	11	10
00	1	1	0	0
01	1	1	1	1
11	0	1	0	0
10	0	1	1	0

$\Rightarrow$

$$F = a'c' + c'd + a'b + ab'd \quad (9)$$

Expand K-Map of F

$ab \backslash cd$	00	01	11	10
00	1	1	0	0
01	1	1	1	1
11	0	1	0	0
10	0	1	1	0

$\Leftarrow$

It would not be reduced again as it has reached local optimum(9). Further reducing would increase literal again.

Irredundant

K-Map of F

$ab \backslash cd$	00	01	11	10
00	1	1	0	0
01	1	1	1	1
11	0	1	0	0
10	0	1	1	0

Nothing to remove

$\Downarrow$

Reduce

K-Map of F

$ab \backslash cd$	00	01	11	10
00	1	1	0	0
01	1	1	1	1
11	0	1	0	0
10	0	1	1	0

$$F = a'c'd' + c'd + a'bc + ab'cd \quad (12)$$